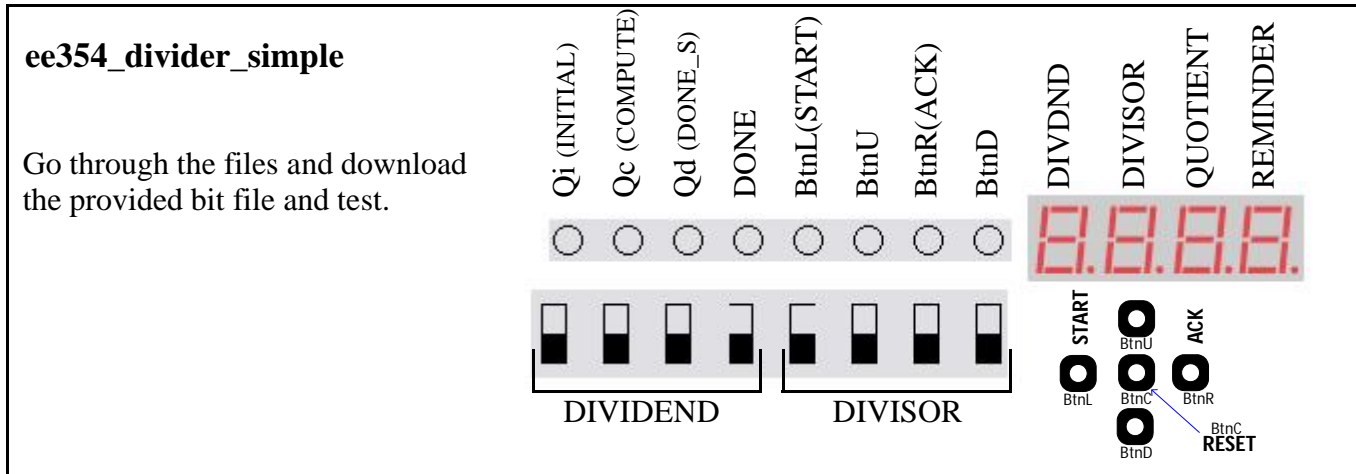



EE354L

Divider RTL design in Verilog

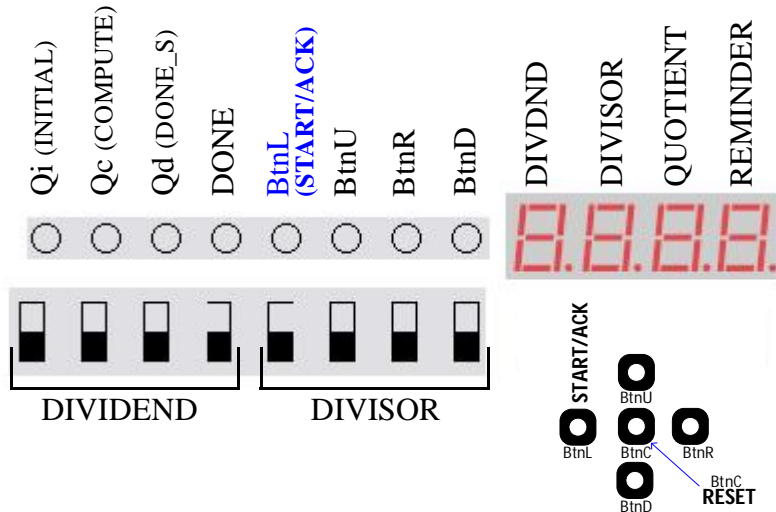Questions for the ee354_divider_simple design:



Note that, unlike in the earlier design, (**ee354_divider_simple**), we run the core divider in this design at the **full speed of 100Mhz**.




2. When you simulate, zoom into the area of the above waveform extract and arrive at your answer for the above question in the waveform extract (why do we see 8 more pulses on MCEN after already seeing two pulses).

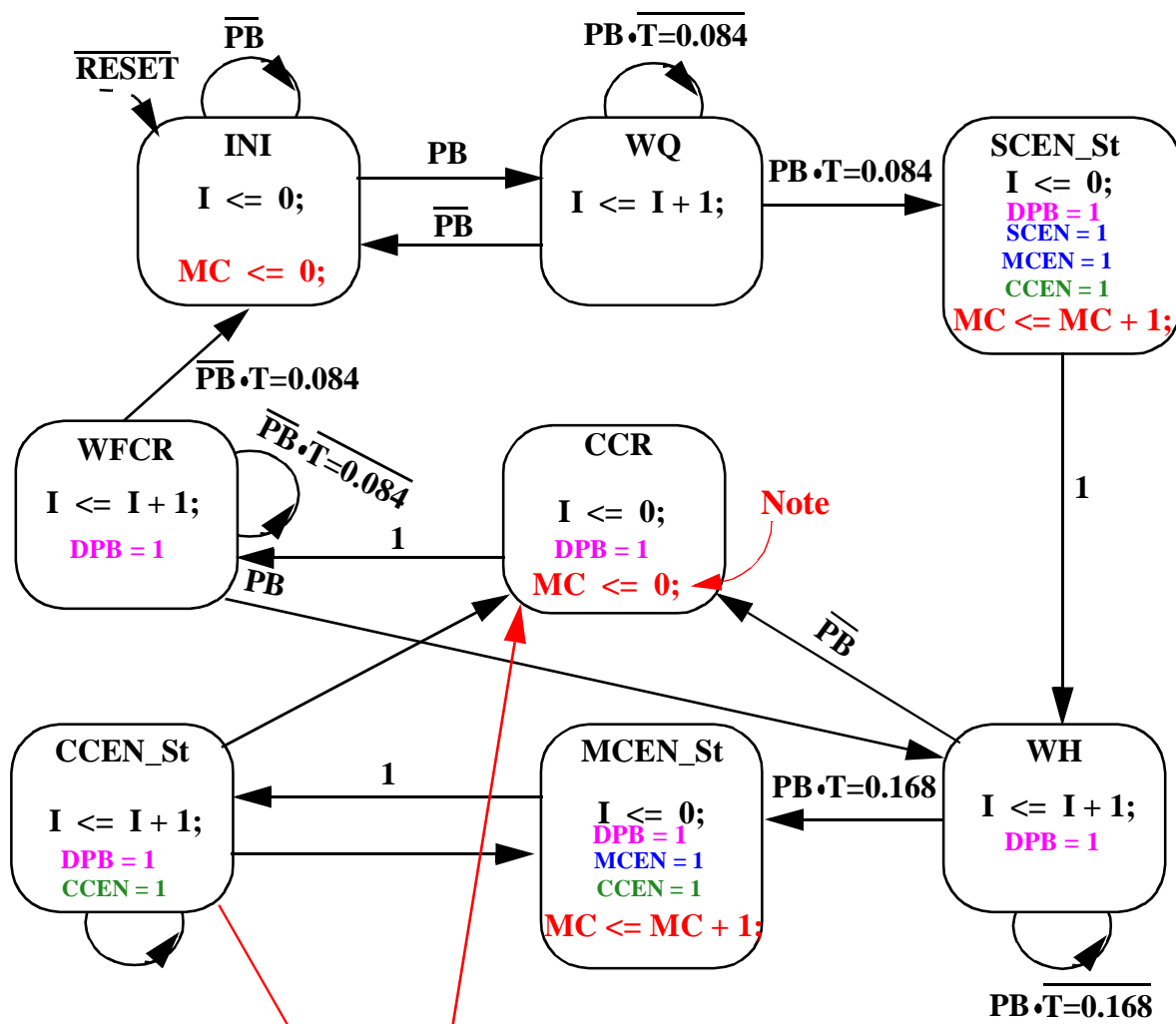3. Did we use the DPB (Debounced Push-Button) pulse or SCEN (Single-Clock enable) pulse to act as the Start signal and the Acknowledge signal? Could we have used anyone of them?

Read the code (ee254_debounce_DPB_SCEN_CCEN_MCEN.v) and complete the state diagram below.


Complete the Debouncing State Machine with the added state MCEN_cont
Complete the missing state transition conditions and also any RTL in the state MCEN_Cont



MC stands for MCEN count.
After certain count of MCN,
control is transferred to
MCEN_Cont.

MCEN_Continuous state
 Here MCEN behaves like CCEN.
 See the output coding table given before.

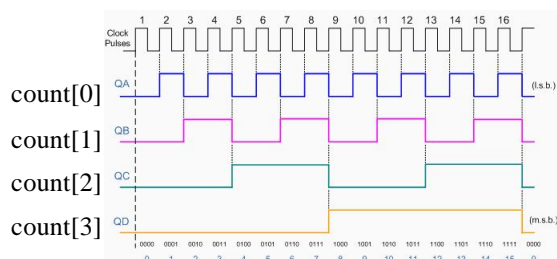Nexys 3 board clock is at 100MHz.
 100MHz frequency corresponds to 10ns clock period.




count[3] becomes 1 after 8 ($=2^3$) clocks of the CLOCK.
 count[2] becomes 1 after 2^2 clocks of the CLOCK.
 2^3 clocks each of 10 ns make 0.084 sec. Hence $T_1 = 0.084$ sec
 2^4 clocks each of 10 ns make 0.168 sec. Hence $T_2 = 0.168$ sec

Names of the students submitting:

- 1.
- 2.
- 3.

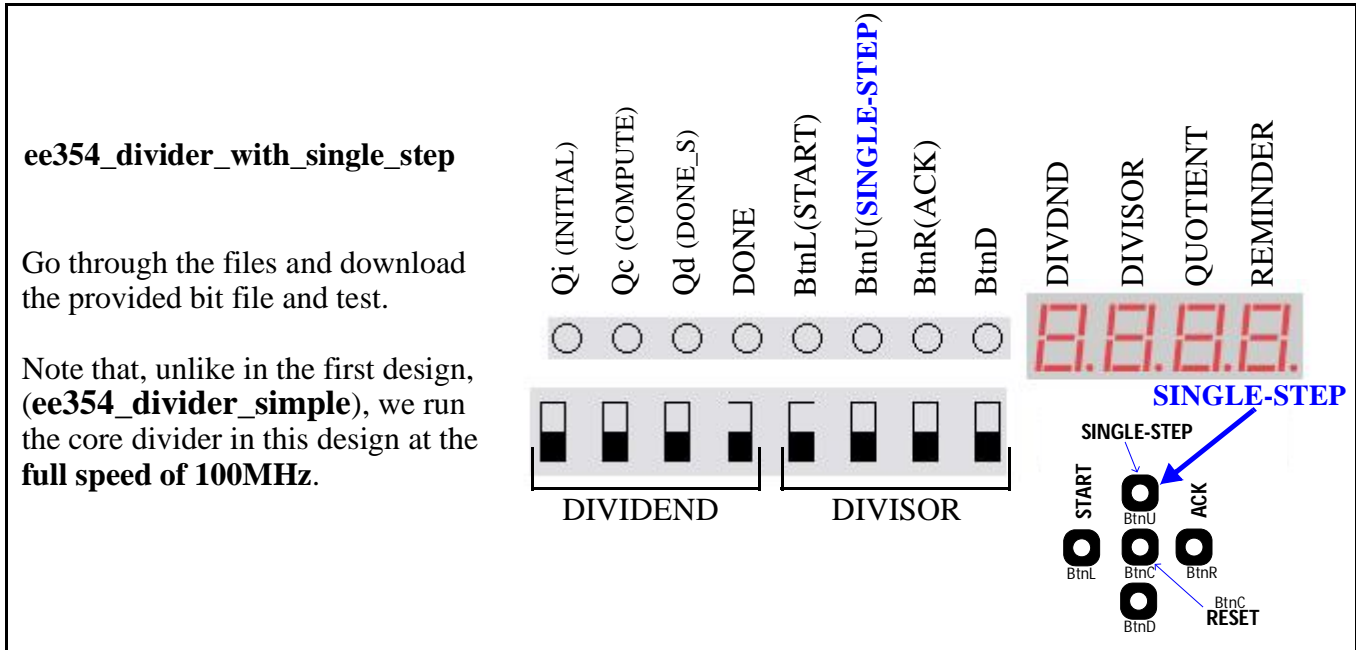
Questions on ee354_divider_with_single_step:



A. Is it possible to use SCEN to control one state (or a few states), MCEN to control another state, and further CCEN to control yet another state? When we say “control a state” here, we mean control the RTL operations in the state and also the state-transitions going away from the state (excluding looping-around state transitions). If we are not going away from the state (because of absence of the SCEN pulse) then we will remain in the state, whether originally there is a loop-around state-transition or not.

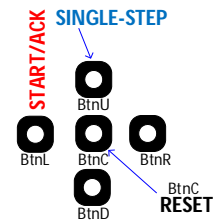B. Can we choose to place **all three states** of the divider design under single-stepping control and *simultaneously* combine Start and Ack under one button (say BtnL)? Is this just not possible or it works if we produce a BtnL_ SCEN and use it as START as well as ACK, or ...?

Can you press two buttons exactly at the same time to 10ns or 5ns accuracy? Even if you press at the same time to that accuracy, can you guarantee that they bounce for the same length of time and the two instances of the debouncing state machine would produce their respective SCEN pulses at the same time?



C. We took time to design output-coded state machine with no OFL at all, there by avoiding any glitches in the SCEN, MCEN, etc. Are glitches really harmful in our design or we have just shown a way to produce glitch-free outputs?
